

EENG 5560HW 3 Report Template

Name: Hari krishna

Gonemadata(11642136)

Due: 02/15/2024


Table of Contents

Design.....	3
Block diagrams	3
Overall design.....	3
Subcomponents.....	4
Design explanation	6
Functionality	6
Results.....	7
Generated Schematics.....	7
Waveforms.....	11
Table/Calculations	13
Overall Design	13

Design

Block diagrams

Overall design

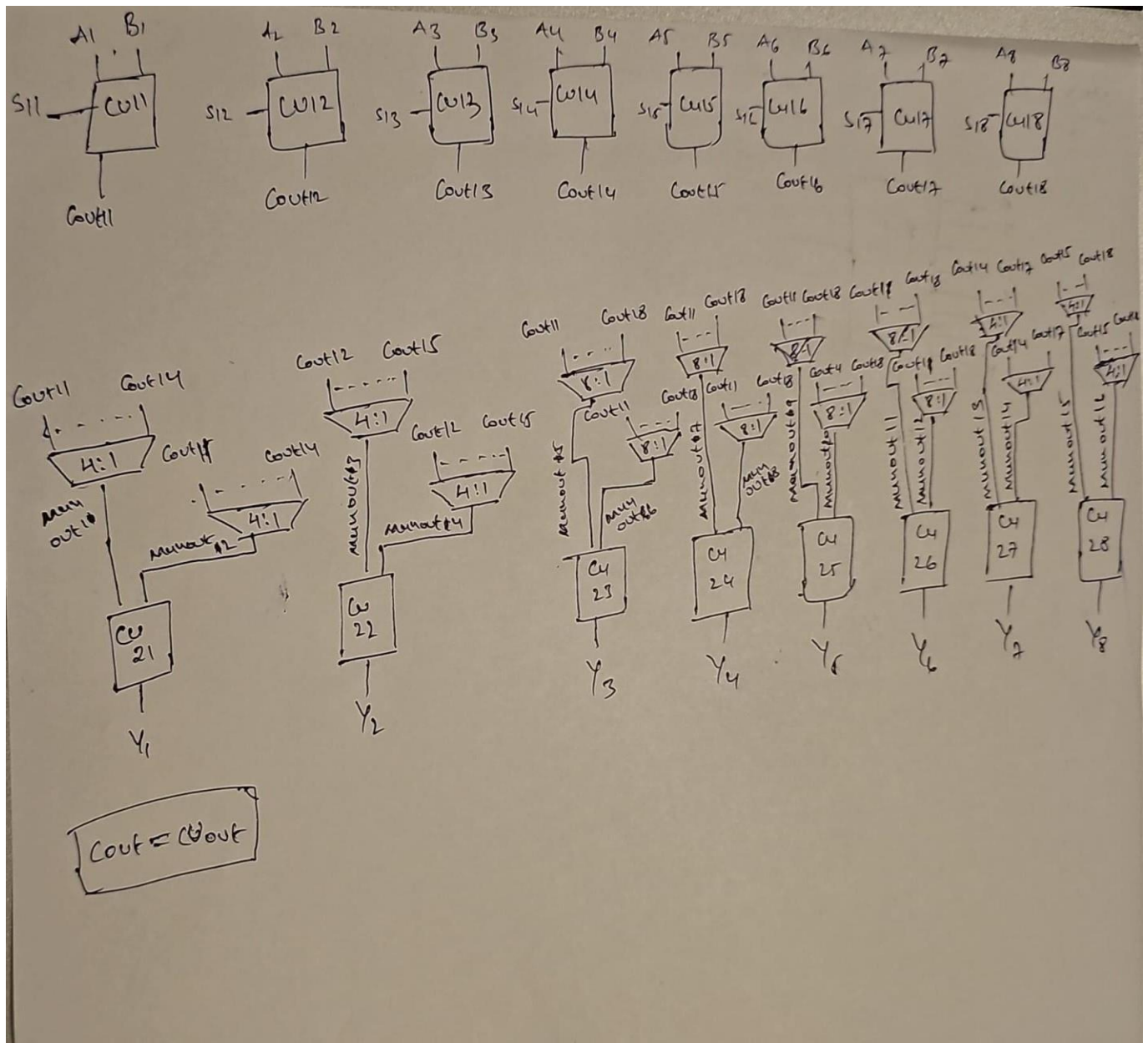

Overall component: top box

Parameters: dw – data width (for inputs and outputs)

Input ports:

Port name	Bit width	Purpose
A1,A2,A3,A4,A5,A6,A7,A8 B1,B2,B3,B4,B5,B6,B7,B8	dw = 4	Data inputs
S11,S12,S13,S14,S15,S16,S17,S18 S21,S22,S23,S24,S25,S26,S27,S28	5	Selection line, selects data input to send to output

Output ports:


Port name	Bit width	Purpose
Y1,Y2,Y3,Y4, Y5,Y6,Y7,Y8	dw = 4	Data output

Necessary intermediate signals:

Port name	Bit width	Purpose
Cuout11- Cuout18, Cuout21- cuout28,	4	Connection between CUs output and Mux input
Muxout 1- muxout16	4	Connection between mux out put and cu's input

Subcomponents

Subcomponent: Computational Unit (CU)

 


Input ports:

Port name	Bit width	Purpose
A	4	DATA INPUTS
B	4	DATA INPUTS
S	5	Selection line

Output ports:

Port name	Bit width	Purpose
O	dw = 4	Data output

Subcomponent: 4 to 1mux:

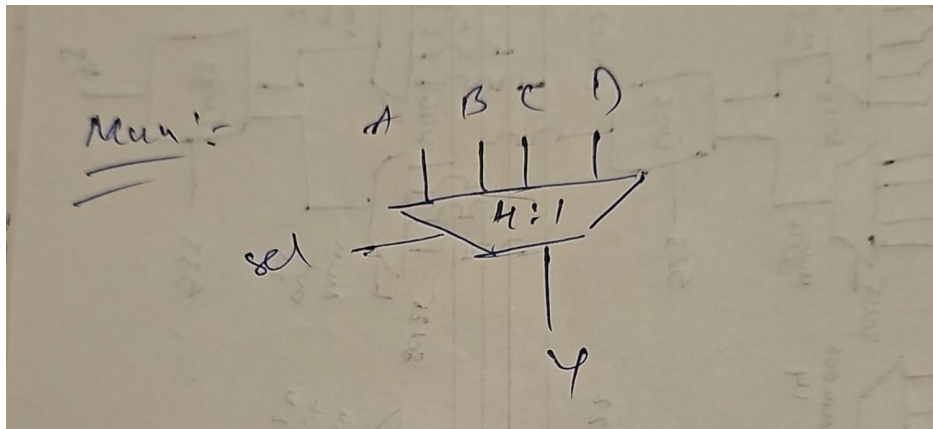


input

Port name	Bit width	Purpose
A,B,C,D	dw = 4	Data inputs
Sel	2	Select line, selects which of the 4 data inputs to send to data output

Output ports:

Port name	Bit width	Purpose
Y	dw = 4	Data output

SUB COMPONENT : 8 to 1 mux:

 

Port name	Bit width	Purpose
A,B,C,D,E,F,G,H	dw = 4	Data inputs
Sel	2	Select line, selects which of the 4 data inputs to send to data output

Output ports:

Port name	Bit width	Purpose
Y	dw = 4	Data output

Design explanation

Functionality

Top box is designed in 8:2 matrix form.

A1 to A8 & B1 to B8 are initial inputs for the CUs in the first row .the output of the CUs send through intermediate signal (cuout 11to cuout18) to muxs.


We are using 4 to 1 and 8 to 1 mux . The outputs of the 1st row CU's are connected to the inputs of the muxes.Output of the muxes are connected as the inputs of the cu's in 2nd row.


Output of the cu's in the 2nd row as main output.


Results

Generated Schematics


Top box:

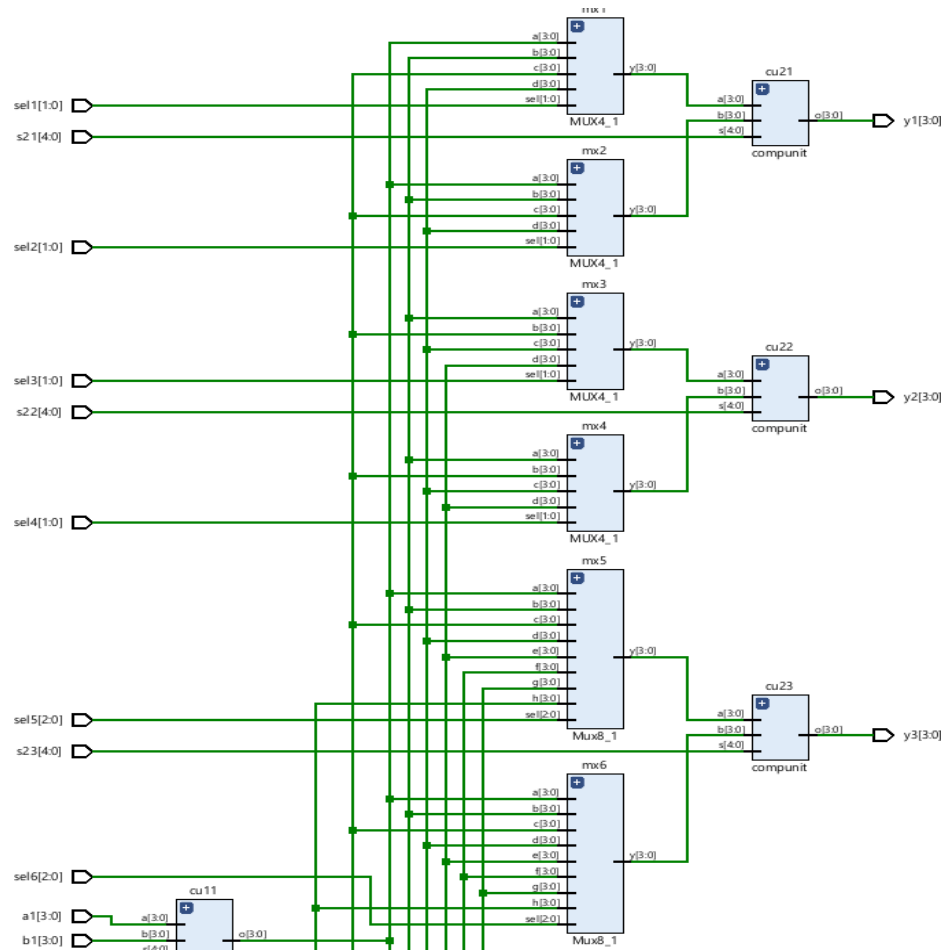

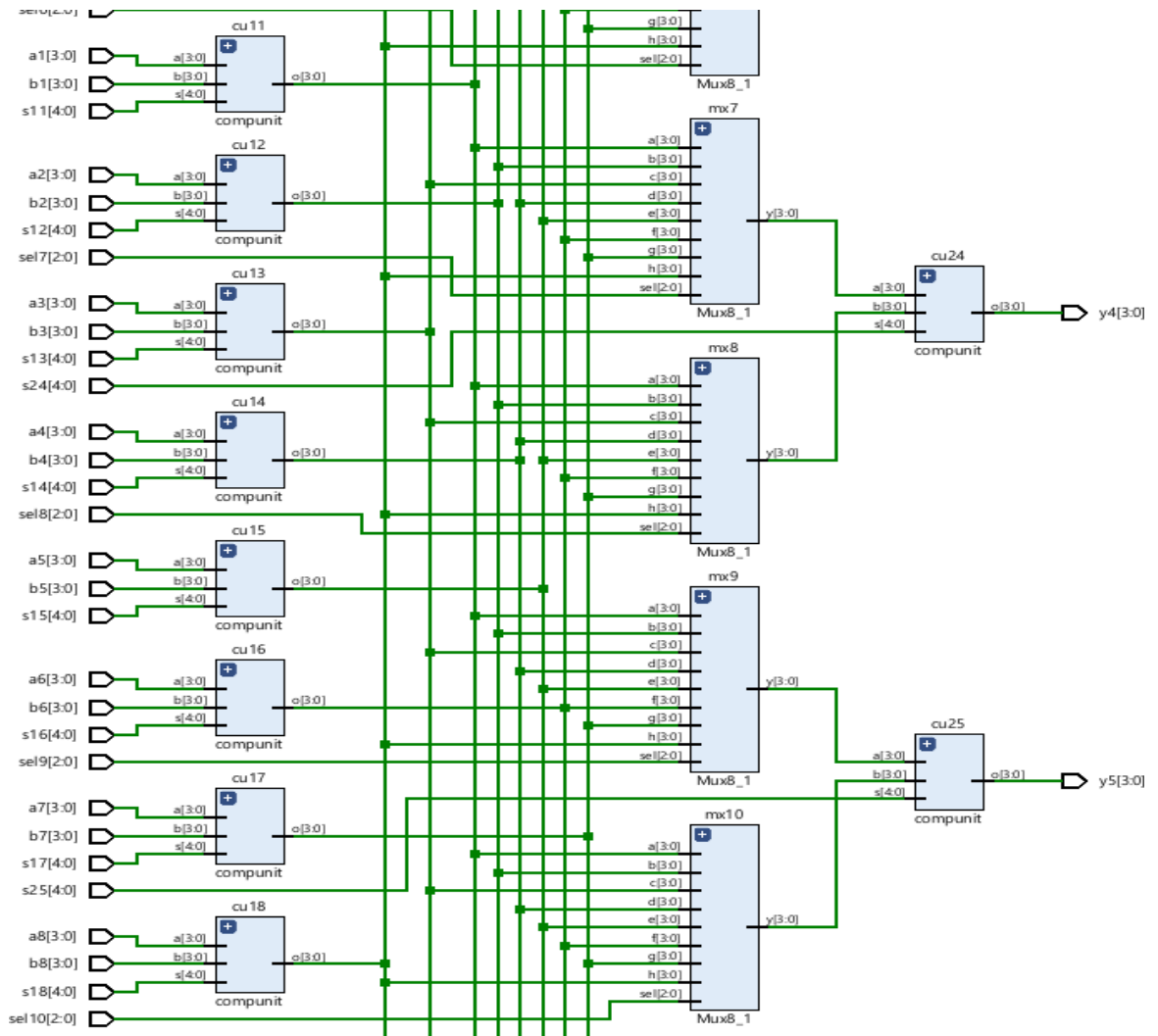


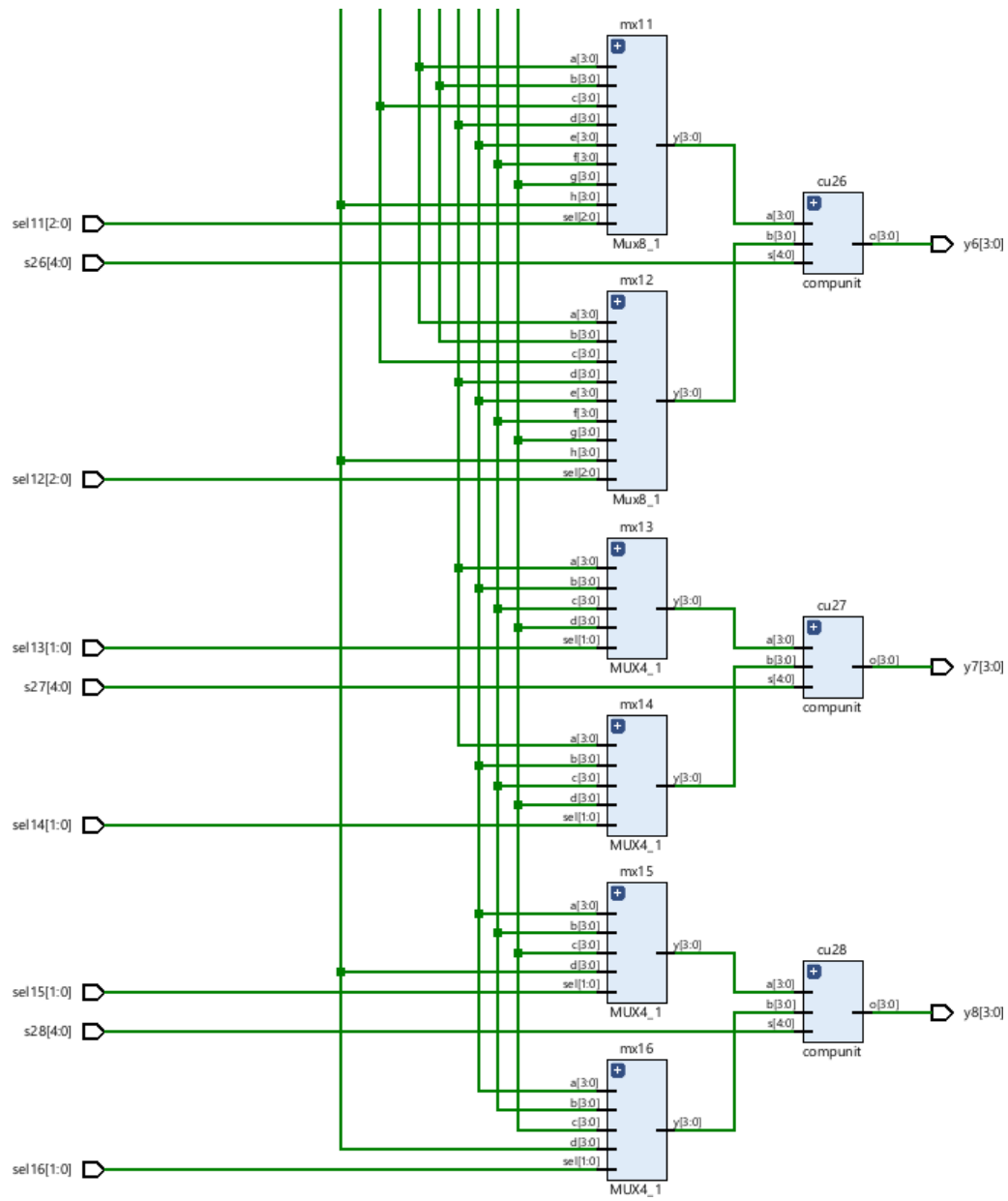


RTL for CU:

 


RTL for 4 to1 mux:

 

RTL for 8 to 1 mux:

 

Waveforms

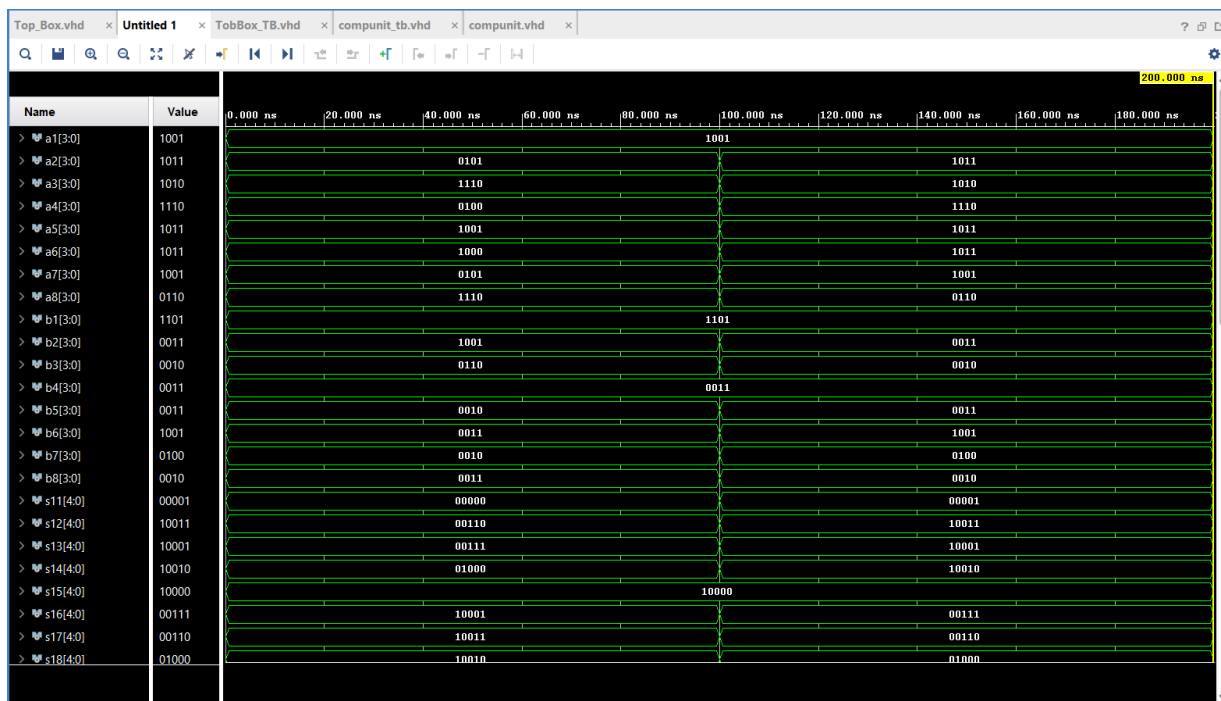

		200.000 ns									
Name	Value	0.000 ns	20.000 ns	40.000 ns	60.000 ns	80.000 ns	100.000 ns	120.000 ns	140.000 ns	160.000 ns	180.000 ns
> s16[4:0]	00111			10001					00111		
> s17[4:0]	00110			10011					00110		
> s18[4:0]	01000			10010					01000		
> s21[4:0]	01001			01100					01001		
> s22[4:0]	10100					10100					
> s23[4:0]	00100					00100					
> s24[4:0]	10101					10101					
> s25[4:0]	01010			01101					01010		
> s26[4:0]	00011					00011					
> s27[4:0]	00010					00010					
> s28[4:0]	01110			01011					01110		
> sel1[1:0]	10			00					10		
> sel2[1:0]	11			01					11		
> sel3[1:0]	10					10					
> sel4[1:0]	00			11					00		
> sel13[1:0]	11			01					11		
> sel14[1:0]	00			10					00		
> sel15[1:0]	00			10					00		
> sel16[1:0]	11					11					
> sel5[2:0]	000			010					000		
> sel6[2:0]	100			110					100		
> sel7[2:0]	110			100					110		
> sel8[2:0]	010			101					010		
> sel9[2:0]	011			001					011		

		200.000 ns									
Name	Value	0.000 ns	20.000 ns	40.000 ns	60.000 ns	80.000 ns	100.000 ns	120.000 ns	140.000 ns	160.000 ns	180.000 ns
> sel4[1:0]	00			11					00		
> sel13[1:0]	11			01					11		
> sel14[1:0]	00			10					00		
> sel15[1:0]	00			10					00		
> sel16[1:0]	11					11					
> sel5[2:0]	000			010					000		
> sel6[2:0]	100			110					100		
> sel7[2:0]	110			100					110		
> sel8[2:0]	010			101					010		
> sel9[2:0]	011			001					011		
> sel10[2:0]	101			111					101		
> sel11[2:0]	111			011					111		
> sel12[2:0]	001			100					001		
> y1[3:0]	1111			0000					1111		
> y2[3:0]	0001			1001					0001		
> y3[3:0]	0010			1100					1111		
> y4[3:0]	0111			1011					0111		
> y5[3:0]	1111			0000					1111		
> y6[3:0]	0011			0000					0011		
> y7[3:0]	1110			1000					1110		
> y8[3:0]	1111			0000					1111		
dw	4					4					

Table/Calculations

Overall Design

Test Case 1 (*0ns to 100ns*):

CU	source a	source b	operation	calculated output	simulated output	matched
CU11	1001	1101	AND	1001	1001	YES
CU12	0101	1001	ADD	1110	1110	YES
CU13	1110	0110	SUB	1000	1000	YES
CU14	0100	0011	MULT	1100	1100	YES
CU15	1001	0010	ASL	0111	0111	YES
CU16	1000	0011	ASR	1111	1111	YES
CU17	0101	0010	LSL	0100	0100	YES
CU18	1110	0011	LSR	0001	0001	YES
CU21	CU11	CU12	GTE	0000	0000	YES
CU22	CU14	CU15	ROR	1001	1001	YES
CU23	CU13	CU17	XOR	1100	1100	YES
CU24	CU15	CU16	ROL	1011	1011	YES
CU25	CU12	CU18	LTE	0000	0000	YES
CU26	CU14	CU15	NOR	0000	0000	YES
CU27	CU15	CU16	NAND	1000	1000	YES
CU28	CU17	CU18	EQ	0000	0000	YES

Test Case # (*100ns to 200ns*):

CU	source a	source b	operation	calculated output	simulated output	matched
CU11	1001	1101	OR	1101	1101	YES
CU12	1011	0011	LSL	1000	1000	YES
CU13	1010	0010	ASR	1110	1110	YES
CU14	1110	0011	LSR	0001	0001	YES
CU15	1011	0011	ASR	1111	1111	YES
CU16	1011	1001	SUB	0010	0010	YES
CU17	1001	0100	ADD	1101	1101	YES
CU18	0110	0010	MULT	1100	1100	YES
CU21	CU13	CU14	GT	1111	1111	YES
CU22	CU14	CU12	ROR	0001	0001	YES
CU23	CU11	CU15	XOR	0010	0010	YES
CU24	CU17	CU13	ROL	0111	0111	YES
CU25	CU14	CU16	LT	1111	1111	YES
CU26	CU18	CU12	NOR	0011	0011	YES
CU27	CU17	CU14	NAND	1110	1110	YES
CU28	CU15	CU18	NEQ	1111	1111	YES